

## Microcontroller controls analog phase shifter

10-21-2020

[Analog Devices](#) > [AD5227](#)

Nick Ierfino

EDN

Phase shifters find use in a variety of circuits, but variation in amplifier and capacitance tolerances usually makes it difficult to control the exact phase shift that precise control circuitry requires. The circuit in Figure 1 can control the phase shift from input to output by using IC<sub>3</sub>, an [AD5227](#) 64-step-up/step-down control digital potentiometer, to replace the value for the resistance. The formula of the center frequency of the output is

$$F_{\text{CENTER}} = \frac{1}{2\pi RC}$$

Slices ▾

• [Microcontrollers](#)

• [e-Newsletter Subscription](#)

• [Contacts](#)



• [Privacy Policy](#)

• [Change Privacy Settings](#)

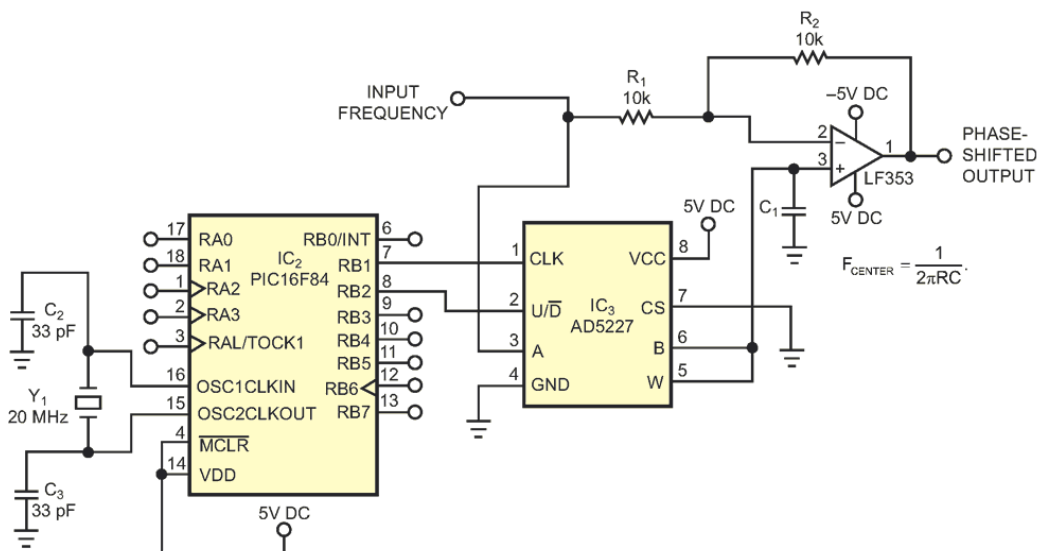


Figure 1. A PIC16F84 sets the resistance of the AD5227 digital potentiometer, precisely controlling the phase shift of the output with respect to the analog input.

Different ranges of resistance are available for the AD5227. This example uses a 10-kΩ value. By stepping through the 64 points, the 720-kHz input sine wave rotates several times from 0 to 360°. The AD5227 acts as a potentiometer, in which A and B are the extremes and W is the wiper.

This example uses IC<sub>2</sub>, a [PIC16F84](#) microcontroller with a crystal frequency of 20 MHz. This microcontroller has a theoretical potential performance of 5 MIPS

and should serve many purposes in PLL (phase-locked-loop) circuitry. You could use any microcontroller or even an FPGA to control the AD5227.

## Materials on the topic

1. [Datasheet Analog Devices AD5227](#)
2. [Datasheet STMicroelectronics LF353](#)
3. [Datasheet Microchip PIC16F84](#)



**Subscribe e-Newsletter to Stay Informed on New Materials of Our Website!**

You may have to [register](#) before you can post comments and get full access to forum.

User Name  ☐ Remember Me?  
Password

Related publications ↓

- [Circuits](#) > [Use Variable DC Voltage To Control 70-MHz Output Phase Shifter](#)
- [News](#) > [Renesas Electronics Announces Dedicated Single-Chip Microcontroller for Single-Phase Static Electricity Meters – 78K0R/LG3-M](#)
- [Datasheets](#) > [Datasheet Analog Devices AD5227](#)
- [Circuits](#) > [Circuit Controls Two LEDs With One Microcontroller Port Pin](#)
- [News](#) > [Texas Instruments Introduces Two-Phase Interleaved CCM PFC Controller – UCC28070](#)